HLS LAB#A Presentation

Team 8


陳昱銓 陳冠豪 楊焌佑

https://github.com/ian861226/ACA21-HLS-LAB-A-team-8

Outline

- 6.5. Accumulator
- 6.6. Shifters
- 6.7. Adder Trees
- 6.8. Lookup Tables(LUT)

Hardware

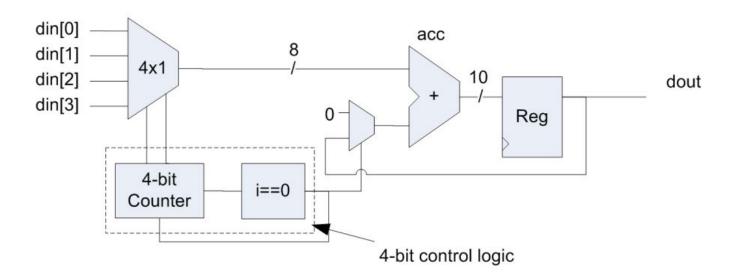

- Design a templatized accumulator with 3 arguments
- W(width): bit width of the input
- S(sign): use signed or unsigned data type
- N(length of array)
- The number of extra bits needed to avoid overflow is log2ceil(N) bits.
 - O Bit width of output

Header

```
const int Width = 8;
const int Num_reg = 4;
const int log2_Num_reg = 2;

template<int W, int N, int l>
ap_int<W + l> acc_tmpl(ap_int<W> din[N]) {
    ap_int< W + l> acc;
    acc = 0;
    ACCUM: for (int i = 0; i < N; ++i)
        acc += din[i];
    return acc;
}

void accumulator(ap_int<Width> din[Num_reg], ap_int<Width + log2_Num_reg>* dout);
```

• Note: Variable used as template argument must be constant in compile time, or synthesis will be failed.


Top function

```
void accumulator(ap_int<Width> din[Num_reg], ap_int<Width + log2_Num_reg>* dout) {
    *dout = acc_tmpl<Width, Num_reg, log2_Num_reg>(din);
}
```


- Test bench
 - Randomly generate 1000 cases, and compare the results.

Accumulator: Utilization

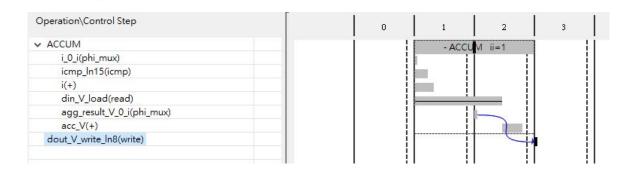Utilization Estimates Summary BRAM_18K Name DSP48E LUT URAM DSP Expression 0 39 FIFO Instance Memory Multiplexer 54 Register 19 Total 19 0 Available 0 280 220 106400 53200 Utilization (%) 0 ~0 0



Accumulator: Waveform

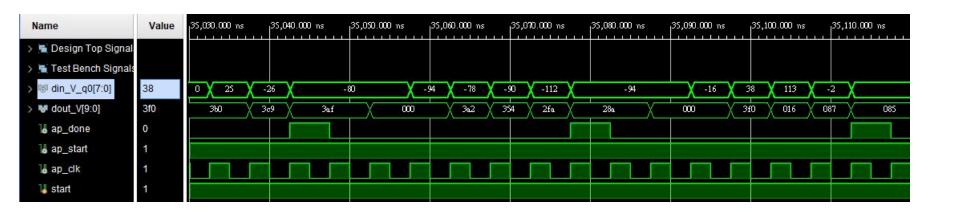

Extension of Accumulator

To design a signed value templatized accumulator

```
template<int W, template<int W2> class dType >
class CData
public:
    dType<W> Content;
template<int W>
class signed ap
public:
    ap int<W> val;
template<int W>
class unsigned ap
public:
    ap uint<W> val;
};
```

```
template<template<int W2> class T, int W, int N, int l>
CData<W + 1, T> acc_tmpl(CData<W, T> din[N]) {
    CData<W + 1, T> acc;
    acc.Content.val = 0;
    ACCUM: for (int i = 0; i < N; ++i)
        acc.Content.val += din[i].Content.val;
    return acc;
}</pre>
```

Extension of Accumulator

Pass csim and csynth, but something strange in cosim...

```
template<int W, template<int W2> class dType >
class CData
public:
    dType<W> Content;
                                                  apatb accumulator.cpp:37:47: error: wrong number of template arguments (2, should be 1)
};
                                                            template<> struct CData<8, signed ap> {
           In accumulator.h
                                                  apatb accumulator.cpp:36:36: note: provided for 'template<int W> struct CData'
                                                            template< int W > struct CData;
#pragma pack()
         template< int W > struct CData;
                                                                               Error message
         template<> struct CData<8, signed ap> {
             signed ap<8 > Content;
         In apath accumulator.cpp
extern void AESL WRAP accumulator (
struct CData<8 > din[4],
ap int<10>* dout);
        In apatb accumulator.h
```

Arithmetic barrel shift : use ap_int

```
ap_int<NUM_BITS> barrel_shift_al(ap_int<NUM_BITS> din, ap_uint<CTRL_BITS> s) {
    return din << s;
}
ap_int<NUM_BITS> barrel_shift_ar(ap_int<NUM_BITS> din, ap_uint<CTRL_BITS> s) {
    return din >> s;
}
```

Logical barrel shift : use ap_uint

```
ap_uint<NUM_BITS> barrel_shift_ll(ap_uint<NUM_BITS> din, ap_uint<CTRL_BITS> s) {
    return din << s;
}
ap_uint<NUM_BITS> barrel_shift_lr(ap_uint<NUM_BITS> din, ap_uint<CTRL_BITS> s) {
    return din >> s;
}
```

Rotating

```
ap_uint<NUM_BITS> barrel_shift_rr(ap_uint<NUM_BITS> din, ap_uint<CTRL_BITS> s) {
    ap_uint<4> stmp = s % NUM_BITS;
    return (din >> stmp) | (din << (NUM_BITS-stmp));
}</pre>
```

Constant shifter

```
ap_uint<NUM_BITS> barrel_shift_lr_const(ap_uint<NUM_BITS> din, ap_uint<CTRL_BITS> s) {
    ap_uint<NUM_BITS> tmp = din;
    if(s == 1)
        tmp >>= 1;
    else if(s == 5)
        tmp >>= 5;
    return tmp;
}
```

Bi-directional

```
ap_uint<NUM_BITS> bi_shift(ap_uint<NUM_BITS> din, ap_int<CTRL_BITS> s) {
    return din >> s;
}

• Example:
    input: 1000 1001 (137)
        s: -1
        output: 0001 0010 (18)
```

Dynamic bit masking: use more operation resources

```
ap_uint<NUM_BITS> shift_mask_dynamic(ap_uint<NUM_BITS> din) {
    ap_uint<NUM_BITS> acc = 0;
    LOOP: for(int i = 0; i < NUM_BITS; ++i)
        acc += (din >> i) & 1;
    return acc;
}
```

Static bit masking: use more registers

```
ap_uint<NUM_BITS> shift_mask_static(ap_uint<NUM_BITS> din) {
    ap_uint<NUM_BITS> acc = 0;
    ap_uint<NUM_BITS> tmp = din;

LOOP: for(int i = 0; i < NUM_BITS; ++i) {
        acc += tmp & 1;
        tmp >>= 1;
    }
    return acc;
}
```


Name	BRAM_18K	DSP48E	FF	LUT	URAM
DSP	1.5	51	-5	878	. 50
Expression	323	29	0	286	J 29
FIFO	15-12	58	= =	878	. 51
Instance	0	29	78	88	J 29
Memory	15-15	51	= 1	8.78	. 50
Multiplexer	323	29	2]	103	J 25
Register	1.51	51	42	878	58
Total	0	0	120	477	0
Available	280	220	106400	53200	0
Utilization (%)	0	0	~0	~0	0

Name	BRAM_18K	DSP48E	FF	LUT	URAM
DSP		(=1)	878	-	273
Expression	32	1 12	0	267	828
FIFO	8	(2)	878	-	273
Instance	0	84-1	78	88	828
Memory	8	(2)	878	-	273
Multiplexer	32	1 12	323	112	828
Register		(2)	50	-	878
Total	0	0	128	467	0
Available	280	220	106400	53200	0
Utilization (%)	0	0	~0	~0	0

Shifters: Top Function

```
switch(mode) {
case 0:
                                                          s V read(read)
     *dout = barrel shift al(din, s);
                                                          din V read(read)
     break;
                                                         mode V read(read)
                                                         _ln8(switch)
case 1:
                                                                                                      sub In556(-)
                                                                                                      - 3
     *dout = barrel shift ar(din, s);
                                                         sh_V(-)
                                                                                                      break;
                                                        > LOOP2
                                                                                                               - LOOP2 ii.
case 2:
                                                          dout V write In31(write)
     *dout = barrel shift rr(din, s);
                                                         dout V write In28(write)
                                                        > LOOP1
                                                                                                                                   - LOOP1
     break:
                                                          icmp In879(icmp)
case 3:
                                                         icmp_ln879_1(icmp)
     *dout = barrel shift ll(din, s);
                                                         select In64(select)
     break;
                                                         select In879(select)
                                                         dout V write In25(write)
case 4:
                                                         r_V_6(lshr)
     *dout = barrel shift lr(din, s);
                                                          dout V write In22(write)
     break;
                                                         r_V_5(shl)
                                                          dout V write In19(write)
case 5:
                                                         r_V_7(lshr)
     *dout = barrel shift lr const(din, s
                                                         r V 8(shl)
     break;
                                                          ret_V()
case 6:
                                                          dout V write In16(write)
     *dout = shift mask dynamic(din);
                                                         r_V_2(ashr)
                                                          dout_V_write_In13(write)
     break;
                                                         r_V_1(shl)
case 7:
                                                         dout V write In10(write)
     *dout = shift mask static(din);
                                                          shl In790(shl)
                                                          Ishr In808(Ishr)
     break;
                                                         r V(select)
default:
                                                          dout_V_write_In34(write)
     *dout = bi shift(din, s);
     break;
```

Shifters: Waveform

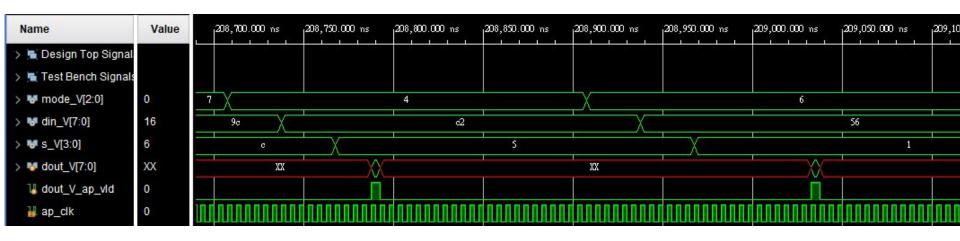


Adder Trees

- Types of adder trees
 - Automatic tree balancing
 - Preventing tree balancing
 - Forcing tree balancing

Adder Trees - automatic tree balancing

Hardware illustration

Code

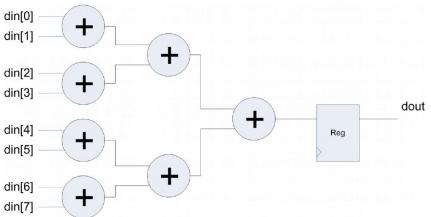


```
#include "Automatic_tree_balancing.h"

ap_int<WIDTH_OUT> adder_tree_balanced (ap_int<WIDTH> din[NUM_REGS] ) {
    #pragma HLS ARRAY_PARTITION variable=din complete dim=1
    #pragma HLS PIPELINE

ap_int<WIDTH_OUT> acc = 0;
adder_loop:for (int i=0; i!=NUM_REGS; i++) {
    #pragma HLS UNROLL
    acc += din[i];
}
return acc;
}
```

Adder Trees - automatic tree balancing

Analysis timeline

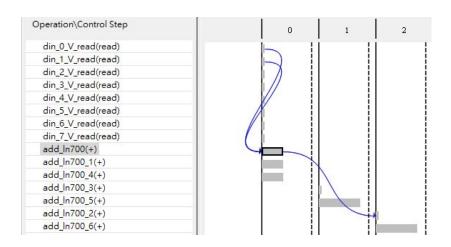

Interface summary

RTL Ports	Dir	Bits	Protocol	Source Object	C Type
ap_clk	in	1	ap_ctrl_hs	adder_tree_balanced	return value
ap_rst	in	1	ap_ctrl_hs	adder_tree_balanced	return value
ap_start	in	1	ap_ctrl_hs	adder_tree_balanced	return value
ap_done	out	1	ap_ctrl_hs	adder_tree_balanced	return value
ap_idle	out	1	ap_ctrl_hs	adder_tree_balanced	return value
ap_ready	out	1	ap_ctrl_hs	adder_tree_balanced	return value
ap_return	out	8	ap_ctrl_hs	adder_tree_balanced	return value
din_0_V	in	8	ap_none	din_0_V	pointer
din_1_V	in	8	ap_none	din_1_V	pointer
din_2_V	in	8	ap_none	din_2_V	pointer
din_3_V	in	8	ap_none	din_3_V	pointer
din_4_V	in	8	ap_none	din_4_V	pointer
din_5_V	in	8	ap_none	din_5_V	pointer
din_6_V	in	8	ap_none	din_6_V	pointer
din_7_V	in	8	ap_none	din_7_V	pointer

Adder Trees - preventing tree balancing

Hardware illustration

Code


#include "Preventing Automatic tree balancing.h"

```
ap int<WIDTH OUT> adder tree unbalanced(ap int<WIDTH> din[NUM REGS], bool s[NUM REGS])
    #pragma HLS INTERFACE ap fifo port=s
    #pragma HLS INTERFACE ap fifo port=din
    ap int<WIDTH OUT> acc = 0;
    ap int<WIDTH> tmp[NUM REGS];
    copied loop:for(int i=0;i!=NUM REGS;i++) {
        #pragma HLS UNROLL
        tmp[i] = din[i];
    operate loop:for(int i=0;i!=NUM REGS;i++) {
        #pragma HLS UNROLL
        if(s[i])
            acc += tmp[i]
    return acc:
```

Adder Trees - preventing tree balancing

Analysis timeline

Interface summary

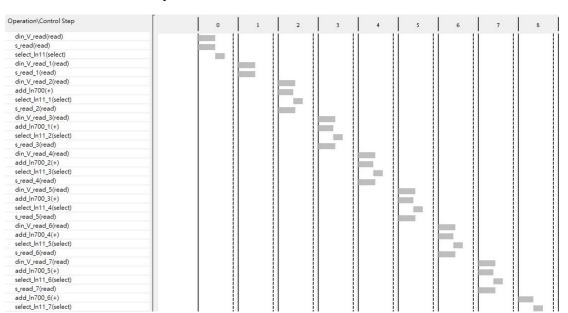


E	CII	100	200	-	-

RTL Ports	Dir	Bits	Protocol	Source Object	СТуре
ap_clk	in	1	ap_ctrl_hs adder_tree_unbalanced		return value
ap_rst	in	1	ap_ctrl_hs	ap_ctrl_hs adder_tree_unbalanced	
ap_start	in	1	ap_ctrl_hs	ap_ctrl_hs adder_tree_unbalanced	
ap_done	out	1	ap_ctrl_hs	adder_tree_unbalanced	return value
ap_idle	out	1	ap_ctrl_hs	ap_ctrl_hs adder_tree_unbalanced	
ap_ready	out	1	ap_ctrl_hs adder_tree_unbalanced		return value
ap_return	out	8	ap_ctrl_hs	ap_ctrl_hs adder_tree_unbalanced	
din_V_dout	in	8	ap_fifo	din_V	pointer
din_V_empty_n	in	1	ap_fifo	din_V	pointer
din_V_read	out	1	ap_fifo	din_V	pointer
s_dout	in	1	ap_fifo s		pointer
s_empty_n	in	1	ap_fifo	ap_fifo s	
s_read	out	1	ap_fifo	ap_fifo s	

Adder Trees - forcing tree balancing

Hardware illustration

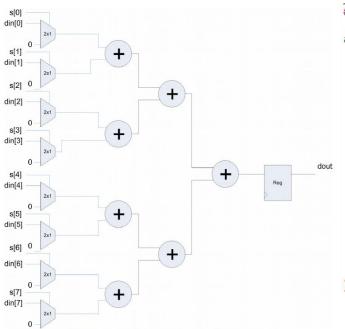


Code

```
#include "Forcing tree balancing.h"
ap int<WIDTH OUT> adder tree rebalanced(ap int<WIDTH> din[NUM REGS], bool s[NUM REGS]){
    #pragma HLS ARRAY PARTITION variable=s complete dim=1
    #pragma HLS ARRAY PARTITION variable=din complete dim=1
    #pragma HLS PIPELINE II=1
    ap int<WIDTH OUT> acc = 0;
    ap int<WIDTH> tmp[NUM REGS];
    copied loop:for(int i=0;i!=NUM REGS;i++) {
        #pragma HLS UNROLL
        tmp[i] = din[i];
    operate loop:for(int i=0;i!=NUM REGS;i++) {
        #pragma HLS UNROLL
        acc += s[i] ? tmp[i] : (ap_int<WIDTH>)0;
    return acc;
```

Adder Trees - forcing tree balancing

Analysis timeline

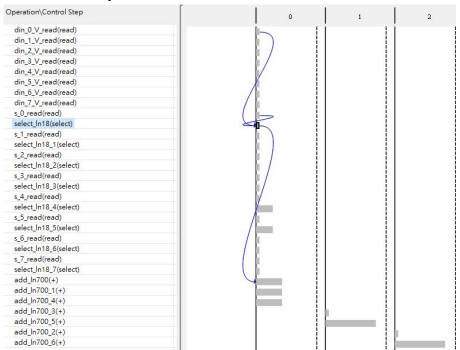

Interface summary

□ Summary

Danniary		L-870-37		5,00, 7,000,000, 80	10000
RTL Ports	Dir	Bits	Protocol	Source Object	СТуре
ap_clk	in	1	ap_ctrl_hs	adder_tree_rebalanced	return value
ap_rst	in	1	ap_ctrl_hs	adder_tree_rebalanced	return value
ap_start	in	1	ap_ctrl_hs	adder_tree_rebalanced	return value
ap_done	out	1	ap_ctrl_hs	adder_tree_rebalanced	return value
ap_idle	out	1	ap_ctrl_hs	adder_tree_rebalanced	return value
ap_ready	out	1	ap_ctrl_hs	adder_tree_rebalanced	return value
ap_return	out	8	ap_ctrl_hs	adder_tree_rebalanced	return value
din_0_V	in	8	ap_none	din_0_V	pointer
din_1_V	in	8	ap_none	din_1_V	pointer
din_2_V	in	8	ap_none	din_2_V	pointer
din_3_V	in	8	ap_none	din_3_V	pointer
din_4_V	in	8	ap_none	din_4_V	pointer
din_5_V	in	8	ap_none	din_5_V	pointer
din_6_V	in	8	ap_none	din_6_V	pointer
din_7_V	in	8	ap_none	din_7_V	pointer
s_0	in	1	ap_none	s_0	pointer
s_1	in	1	ap_none	s_1	pointer
s_2	in	1	ap_none	s_2	pointer
s_3	in	1	ap_none	s_3	pointer
s_4	in	1	ap_none	s_4	pointer
s_5	in	1	ap_none	s_5	pointer
s_6	in	1	ap_none	s_6	pointer
s_7	in	1	ap_none	s_7	pointer

Look Up Table (LUT)

Data

```
Θ,
2 .375,
  .703125,
  .921875,
  .921875,
  .703125,
  .375,
  -.390625,
  -.71875,
  -.9375,
  -1,
  -.9375,
  -.71875,
  -.390625
```


Code

```
#include "lut.h"
ap fixed<WIDTH, 2> lut(ap uint<ADDR WIDTH> i)
  const ap fixed<WIDTH, 2> sin table[NUM REGS] = {
   #include "data.inc"
  return sin table[i];
for(unsigned int i=0;i<NUM REGS;i++) {</pre>
    cout << "-----" << endl:
   golden = sin(2*pi*i/(double)NUM REGS);
   output = lut(i);
   cout << "your output: " << output << endl;
   if(output != golden) {
       cout << "golden: " << golden << endl;
       pass = 0:
       //break;
```

LUT - RTL code

```
`timescale 1 ns / 1 ps
(* rom_style = "distributed" *) module lut_sin_table_rom (
addr0, ce0, q0, clk);
parameter DWIDTH = 8;
parameter AWIDTH = 4;
parameter MEM_SIZE = 16;
input[AWIDTH-1:0] addr0;
input ce0;
output reg[DWIDTH-1:0] q0;
input clk;
(* ram_style = "distributed" * reg [DWIDTH-1:0] ram[0:MEM_SIZE-1
initial begin
    $readmemh("./lut_sin_table_rom.dat", ram);
end
always @(posedge clk)
begin
   if (ce0)
    begin
        q0 <= ram[addr0];
    end
```

LUT - Performance & Interfaces

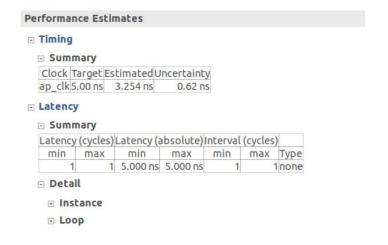

Summary

RTL Ports	Dir	Bits	Prot	ocol	Source Object	СТуре
ap clk	in	1	ар с	trl hs	lut	return value
ap rst	in	1	ар с	trl hs	lut	return value
ap_start	in	1	ap_c	trl_hs	lut	return value
ap_done	out	1	ap_c	trl_hs	lut	return value
ap idle	out	1	ар с	trl hs	lut	return value
ap ready	out	1	ар с	trl hs	lut	return value
ap return	out	8	ар с	trl hs	lut	return value
i_V	in	4	ap	none	i_V	scalar

